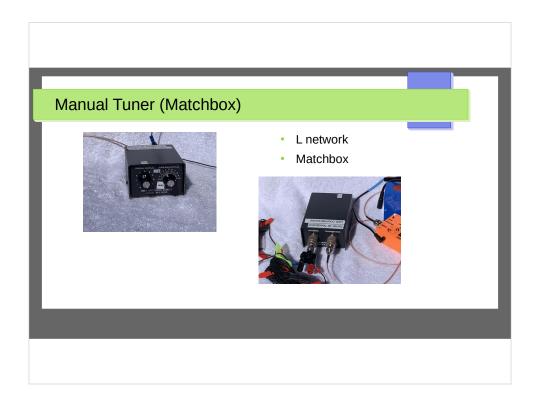


- Have a compact kit, ATU a little big and heavy, needs power, cheap ones are wonky. Small manual preferred but tuning is a little tedious.
- Small autotuners exist
- Curiosity-- is there a different way to do it?




Tuner is compact. One variable capacitor, one inductor with multiple taps. L is in series, C is shunt


In principle will match anything as long as the ranges of values of C & L are large enough.

Sometimes you have to reverse the direction (just by reversing connections) depending on the antenna impedance. Namely whether the native antenna real part is above or below the frequency of interest

In principle one solution

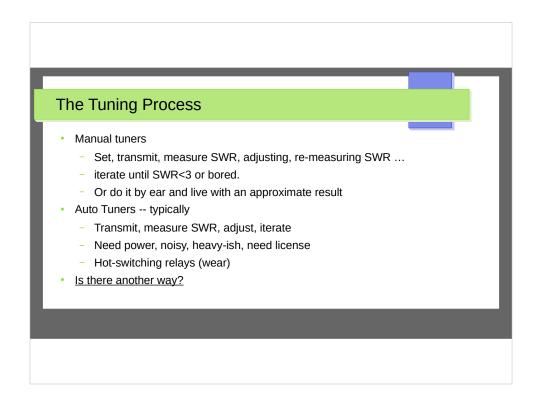


- Some nice little compact auto-tuners out there
- Auto Tuners typically work by transmitting, directly measuring SWR and searching.
  - Requires transmitting
  - Requires a powered tuner with relays etc
- Manual tuners work by setting, measuring SWR, adjusting, re-measuring SWR ... iterate until SWR<3 or bored. Or do it by ear and live with an approximate result.
- Melville and Hamilton took a different approach
  - Characterize the tuner and antenna
  - Calculate result
  - Remotely adjust tuner head with servos and relays

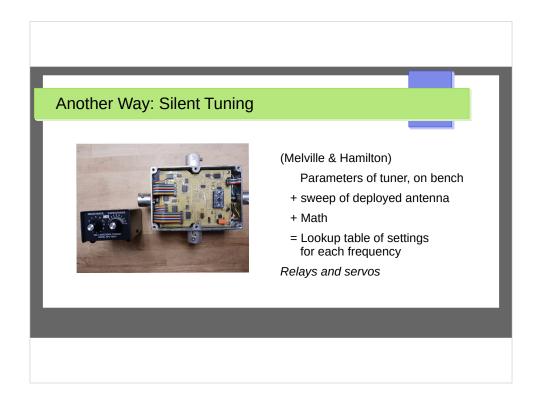


Relays and servos are needed for automation, but what if I'm willing to make the indicated adjustments by hand?
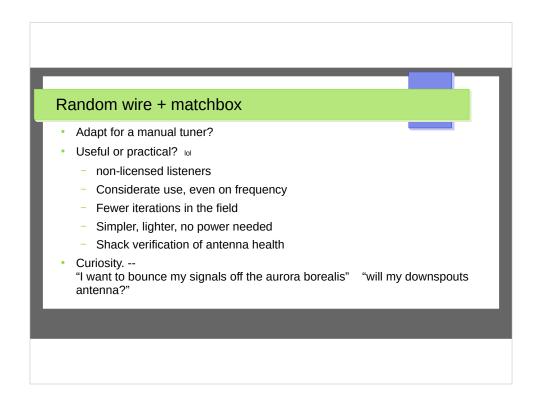
# I could eliminate

- electromechanical complexity
- Weight
- Power requirement



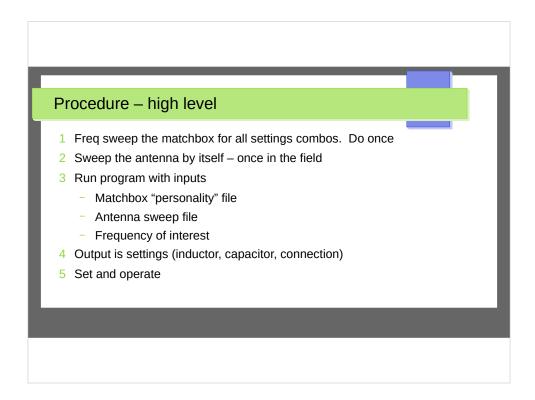No goofier than many other questions we ask as hams




Matchbox personality file: S11, S12, S21, S22 sweep from .8 MHz to 32 MHz

Sweep the antenna in the field, as many points as you like, record S11


This is a summary of the procedural steps. Now let's see details about how it's actually done:



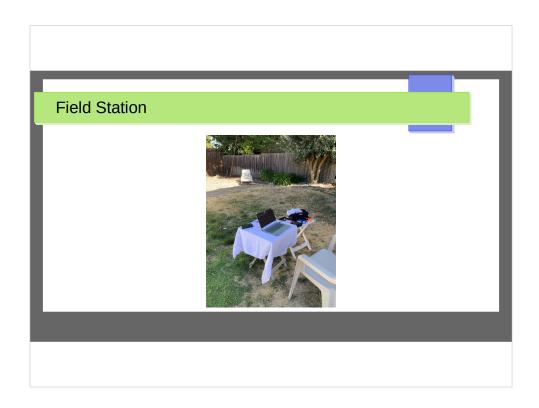
The other BNC connector here goes to the radio




Just FYI what it looks like deployed

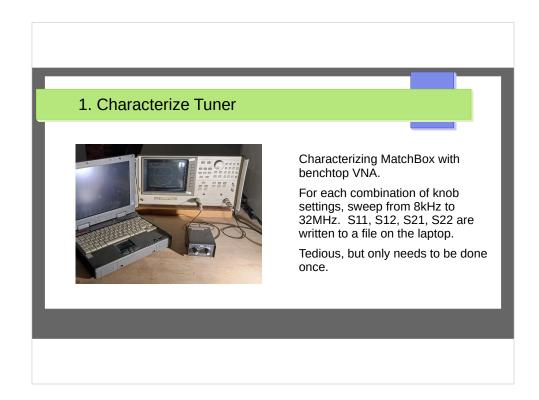


HP 8753D lab VNA, fyi

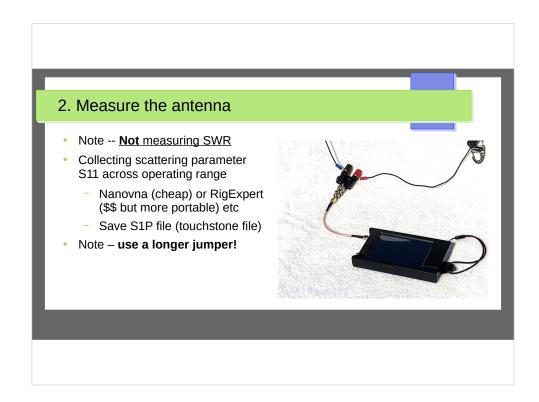

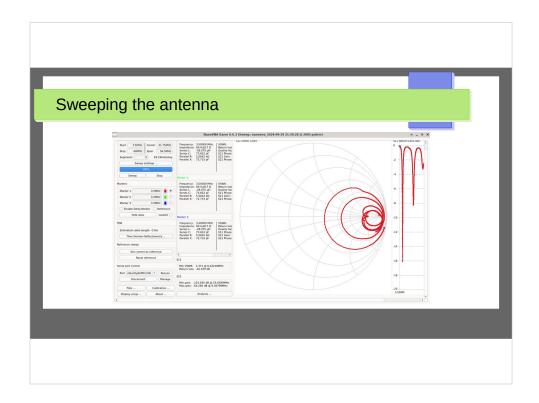When the jumper is this short, your presence interferes with measurments.



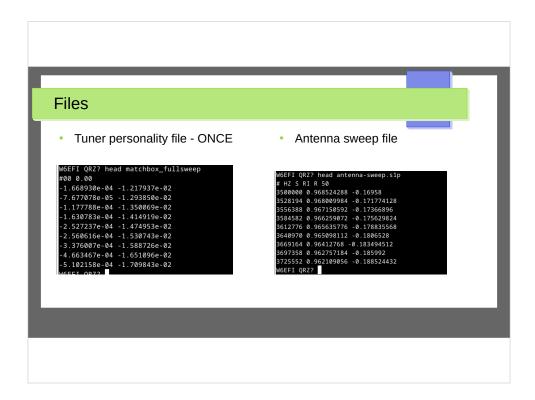- NanoVNASaver
- Set Start and Stop frequencies
- Set "number of segments" high enough to get small enough steps (better resolution). 5 is probably excessive
- Click on "Files" and "save 1-port file" S1P file
- Touchstone file (a text file with descriptive header)



### Explanation of the format of the matchbox "personality" file:

Each combination of settings is preceded by its own # format header Each line corresponds to a frequency -- 801 of them in HZ 8e5 to 32e6 inclusive

The first 801 lines are S11 for that set of frequencies

The next 801 lines are S21 for the same set of frequencies


The third set are S12...


The fourth set are S22 ...

#### Format of the antenna sweep file (Touchstone standard):

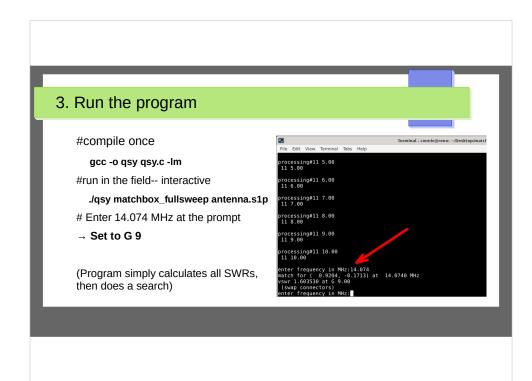
# format header

Frequency (Hz) S11 real part S11 imaginary part



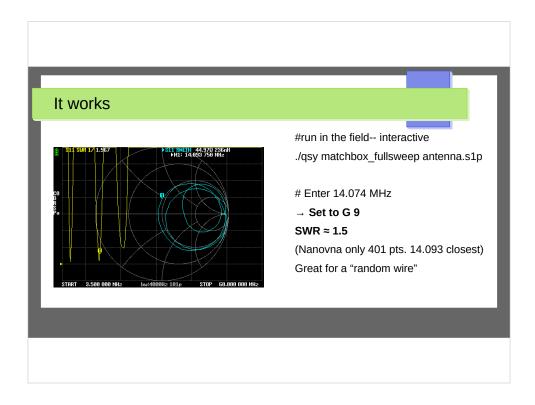

Pretty near the minimum. Resolution

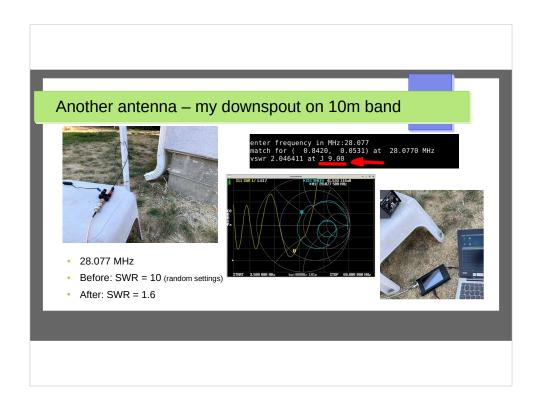

Side note: my downspout and gutters are around 1.5:1 on the 20m band without a tuner so didn't demo there. But it's a good problem to have! I have worked the middle of the country on phone on this downspout with 10 Watts on 20m and no tuner

#### Lessons learned:

MUST take antenna measurements with at least several feet of jumper. DO NOT be right next to the antenna when you measure it. This goes for ALL antennas. Standing near it with your VNA guarantees messed-up measurements

Re NanoVNA + freeware on computer: great little instrument, but you do get what you pay for. Setup occasionally locks up when alternating screenshots and measurements

#### Incidental lessons learned along the way

- Learned that we wanted more capacitance
  - Added a capacitor with a switch.
  - Recharacterized, adjusted search
- Need good connections, reliable connectors and jumpers
- Jumper from NanoVNA to antenna feed point needs to be at least several feet long. Antenna measurements for ANY antenna are unreliable when you are standing right at the feed point
- Can be twitchy depending on how solid your mechanical connections are
- L tuners are simple, one-solution, but narrow bandwidth, adds twitchiness

### Things to do next

- Nomogram or booklet? Ie, no compute in the field?
- Ideal wire length for a given tuner modelling, or measuring
- Put everything in a single box: autotuner that incorporates a VNA/measure S11 plus small compute. Or modular kit.
- Put all the compute on your phone phone will run c or python.
  - Connect phone to VNA, VNA to antenna
  - Run program, set tuner, win contests!

•

# Parting comments – why, even?

- tuning by ear is time-honored tradition...
  - But, it depends on your ear
  - can get you stuck in local minima which we avoid.
  - Tuning by ear can be tedious.
- In the field, being able to start with settings that are close and then just do a minor tweak is a big win.
- Don't have to transmit.
- Less wear.
- No need for ATU power or weight.
- Make big \$\$ selling ham products! loljk (next slide...)



VNA and compute are small and cheap. Why not duct-tape them together, display the settings for the user?

But seriously, instead of a bunch of relays and electromechanical iterative search, put in the guts of a nanoVNA and compute with a small display telling the user what settings to pick. Skip the electromechanicals for weight, space, cost, and tinkerability.

Add servos and relays, and we've circled back to Melville and Hamilton.

# Why even...? ...Ultimately:

Because we're hams, and we like to tinker! -- that's one of the reasons the amateur bands even exist  $% \left\{ 1,2,...,4\right\}$ 

Thanks and have fun!

GE es 73 de W6EFI

### Resources

- Matchbox sweep files (for MFJ 16010 manual tuner)
- Code (yet to be posted contact presenter)
- https://github.com/conniest/InstantTuning

•

# Appendix 1: L-Match Tuner

- · Capacitor and inductor, one in series and one in parallel with antenna
- Which way depends on whether the antenna R is high or low.
- That's why you sometimes reverse the connections.
- In theory should always be able to get a match (limited by cpt values)
- Orientation determines hi-pass or lo-pass

# Format of the matchbox "personality" file

- S11, S12, S21, S22 values over freq range of interest
- Each combination of settings is preceded by its own # format header
- Each line corresponds to a frequency -- 801 of them in Hz: 800kHz to 32MHz inclusive
- The first 801 lines are S11 for that set of frequencies
- The next 801 lines are S21 for the same set of frequencies
- The third set are S12 ...
- The fourth set are S22 ...

# Appendix 3: qsy.c algorithm summary

- Read matchbox "personality" file (S11, S12, S21, S22 for freq range)
- Read antenna sweep file (S11 for freq range)
- Read input frequency
- Do some interpolation for frequency
- $^{\bullet}$  Iterate over all combinations of L & C settings and antenna connected to each port
- · Calculate resultant input reflection coefficient and SWR, save them all in a table
- Search table for lowest SWR
- Print those settings, may include direction to reverse the ports

### Appendix 4: Calculation notes

#### Reflection coefficient $\Gamma$

$$=rac{V_r}{V_f}.$$

$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o}$$

$$SWR = \frac{|V_{\text{max}}|}{|V_{\text{min}}|} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$|\Gamma| = \frac{SWR - 1}{CMR + 1}$$

 $\begin{array}{l} Z_L : \mbox{ load impedance} \\ Z_D : \mbox{ characteristic impedance of feedline} \\ V_L : \mbox{ reflected voltage} \\ V_L : \mbox{ forward voltage} \end{array}$ 

$$s_{\text{in}} = \frac{1 + |S_{11}|}{1 - |S_{11}|}$$

or  $\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o} \\ \text{SWR} = \frac{|V_{\text{max}}|}{|V_{\text{min}}|} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \\ \text{SWR} + \frac{|SWR - 1|}{|SWR + 1|} \\ \text{Sym} = \frac{1 + |\Gamma|}{1 - |S_{21}|} \\ \text{At the output port, the VSWR}(s_{\text{out}}) \text{ is given by}} \\ s_{\text{out}} = \frac{1 + |S_{11}|}{1 - |S_{22}|} \\ \text{Sym} = \frac{1 + |S_{22}|}{1 - |S_{22}|} \\ \text{Sym}$ 

#### Now connect a load (antenna) having $\Gamma_{\text{L}}$ (S\_{\tiny 11ant}) to the output port.

Input reflection coefficient with the output termination arbitrary and  $Z_S = Z_0$ .

nation arbitrary and 
$$c_s = Z_0$$
. 
$$s_{11}' = \frac{b_1}{a_1} = \frac{s_{11}(1 - s_{22}\Gamma_L) + s_{21}s_{12}\Gamma_L}{1 - s_{22}\Gamma_L}$$
$$= s_{11} + \frac{s_{21}s_{12}\Gamma_L}{1 - s_{22}\Gamma_L}$$

SWR looking into the tuner with the antenna attached

$$SWR_{tuner\ with\ ant} = \frac{1 + |S'_{11}|}{1 - |S'_{11}|}$$

#### References

#### Silent tuning

 R. Melville and S. Hamilton, "Silent Tuning: Matching a transmitter to an antenna without emitting a signal," MILCOM 2021 - 2021 IEEE Military Communications Conference (MILCOM), San Diego, CA, USA, 2021, pp. 808-812, doi: 10.1109/MILCOM52596.2021.9653009.

#### Antennas and tuners

- ARRL, The ARRL Antenna Book (24<sup>th</sup> ed)
- Krischke, J., DJ0TR, Rothammel's Antenna Book

#### Scattering parameters, reflection coefficients

- https://en.wikipedia.org/wiki/Scattering\_parameters
- https://people.engr.tamu.edu/spalermo/ecen689/sparam\_agilent\_tutorial.pdf

#### **Author Biographies**

**Connie Stillinger, PhD., W6EFI** Connie was originally licensed in the 1970's as WN2EFI -- passed the 5 wpm code test -- but it lapsed before even making it into the callbook. About two years ago she rediscovered ham radio as a great way to make friends, hike around parks, and have fun tinkering together. She enjoys operating all modes on HF ranging from CW through Hellschreiber to SSTV

Robert Melville, PhD., WB3EFT Bob worked at AT&T Bell Labs for 17 years in the areas of computer-aided design, numerical simulation of electronic circuits, and design and fabrication of RF integrated circuits. He has taught electrical engineering at Columbia University and served with the United States Antarctic Program at the Amundsen-Scott base at the South Pole doing engineering work in support of geophysics experiments. Bob is a Senior Member of the IEEE, who referees for leee-sponsored journals and conferences, and the Society for Industrial and Applied Mathematics. He co-organized a conference on numerical circuit simulation at Sandia National Labs and participated in the AT&T "Teachers and Technology" enrichment program for high-school math and science teachers.